
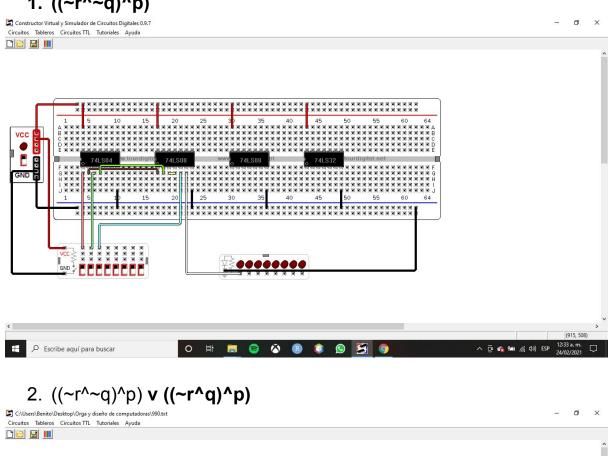
## Tarea 990: Realizar el siguiente ejercicio en el simulador de circuitos digitales


Expresión:  $((\sim r^{\sim}q)^{p})v((\sim r^{q})^{p})v((r^{q})^{\sim}p)v((r^{q})^{p})$ 



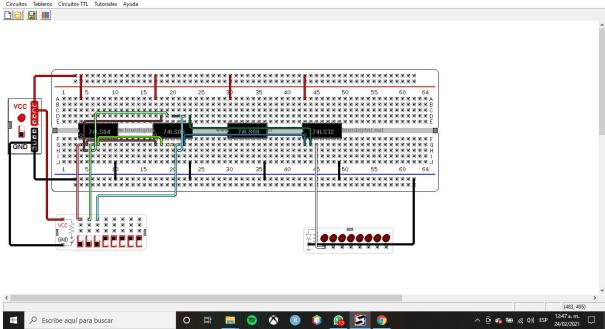



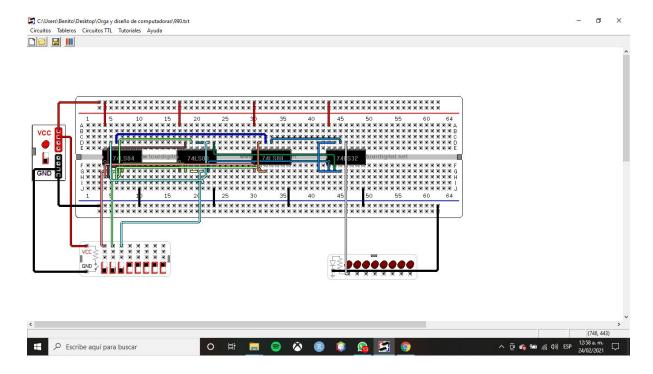3.  $((-r^{-q})^{p}) \vee ((-r^{q})^{p}) \vee ((r^{q})^{-p})$ 



## 4. $((-r^{-q})^{p})v((-r^{q})^{p})v((r^{q})^{-p})v((r^{q})^{p})$

